

---

# FILTERS

---

## NOTES ON PASSIVE ELECTRIC FILTER CIRCUITS

Hannah Michelle Ellis

June 2, 2020

# Contents

<b>1</b>	<b>RC Low Pass Filter</b>	<b>2</b>
1.1	Filter Attenuation . . . . .	2
1.2	Cutoff Frequency . . . . .	4
1.3	Log-Log Plots . . . . .	6

# List of Tables

# List of Figures

1	Circuit diagram for a RC low pass filter. . . . .	2
---	---	---

# 1 RC Low Pass Filter

## 1.1 Filter Attenuation

A simple low pass filter can be formed from a resistor and a capacitor in series.

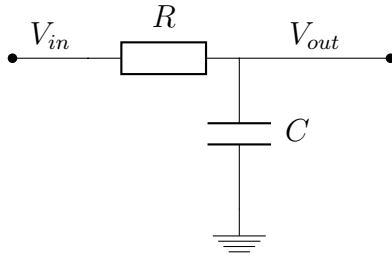


Figure 1: Circuit diagram for a RC low pass filter.

We can see from figure 1, that the output voltage is the same as the voltage across the capacitor. So we have

$$\begin{aligned} V_{in} &= V_R + V_C \\ &= IR + V_{out} \end{aligned} \tag{1.1}$$

Using the fact that the current through the RC section of the circuit is given by

$$I = \frac{V_{in}}{R - iX_C} \tag{1.2}$$

Leading to the output voltage being

$$\begin{aligned} V_{out} &= V_{in} - IR \\ &= V_{in} - \frac{V_{in}R}{R - iX_C} \\ &= V_{in} \left[ 1 - \frac{V_{in}R}{R - iX_C} \right] \end{aligned} \tag{1.3}$$

which leads to a ratio of the output voltage to the input voltage of

$$\begin{aligned}
 \frac{V_{out}}{V_{in}} &= 1 - \frac{R}{R - iX_C} \\
 &= \frac{-iX_C}{R - iX_C} \\
 &= \frac{-iX_C(R + iX_C)}{R^2 + X_C^2}
 \end{aligned} \tag{1.4}$$

Now if we let

$$u = \frac{R}{X_C} = \omega RC \tag{1.5}$$

we can see that  $R = uX_C$ , and putting this in equation 1.4 leads to

$$\frac{V_{out}}{V_{in}} = \frac{-iX_C^2(u + i)}{u^2X_C^2 + X_C^2} \tag{1.6}$$

$$= \frac{1 - iu}{1 + u^2} \tag{1.7}$$

We can work out the magnitude and the phase angle of the attenuation through the filter as follows.

$$\begin{aligned}
 \left| \frac{V_{out}}{V_{in}} \right| &= \sqrt{\frac{1 - iu}{1 + u^2} \frac{1 + iu}{1 + u^2}} \\
 &= \frac{\sqrt{1 + u^2}}{1 + u^2} \\
 &= \frac{1}{\sqrt{1 + u^2}}
 \end{aligned} \tag{1.8}$$

and for the phase factor

$$\begin{aligned}
 \phi &= \arctan \left( \frac{\frac{-u}{1+u^2}}{\frac{1}{1+u^2}} \right) \\
 &= -\arctan u
 \end{aligned} \tag{1.9}$$

## Summary

We looked at the classic example of a low pass RC filter circuit, and discovered the relationship between the voltage into the filter and the voltage out of the filter is given by

$$\frac{V_{out}}{V_{in}} = \frac{1 - iu}{1 + u^2}$$

Or in terms of magnitude and phase angle

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + u^2}}$$
$$\phi = -\arctan u$$

where  $u = \frac{R}{X_C} = \omega RC$ .

## 1.2 Cutoff Frequency

Letting the attenuation  $a = \left| \frac{V_{out}}{V_{in}} \right|$  and rearranging will give us

$$a = \frac{1}{\sqrt{1 + u^2}}$$
$$1 + u^2 = \frac{1}{a^2}$$
$$u = \frac{\sqrt{1 - a^2}}{a} \tag{1.10}$$

Equation 1.10 and 1.5 can be used together to calculate component values if a particular attenuation is required at a particular frequency. However an interesting result is the attenuation when

$$u = 1.$$

$$\begin{aligned}
 u &= 1 \\
 a &= \frac{1}{\sqrt{1+u^2}} \\
 &= \frac{1}{\sqrt{1+1}} \\
 &= \frac{1}{\sqrt{2}}
 \end{aligned} \tag{1.11}$$

When looking at equation 1.5 and considering what it means when  $u = 1$ , you will realise this is when the resistance of the capacitor and the reactance of the capacitor are equal. Also the phase as given by equation 1.9 is  $\phi = -\arctan 1 = -\frac{\pi}{4} = -45^\circ$

The frequency when  $u = 1$  is known as the cutoff frequency of the filter, and is calculated as follows

$$\begin{aligned}
 u &= 1 \\
 2\pi RCf &= 1 \\
 f &= \frac{1}{2\pi RC}
 \end{aligned} \tag{1.12}$$

## Summary

For the RC filter there is a special frequency called the cutoff frequency, which is given by.

We looked at the classic example of a low pass RC filter circuit, and discovered the relationship between the voltage into the filter and the voltage out of the filter is given by

$$f = \frac{1}{2\pi RC}$$

At this frequency both the resistance of the resistor and the reactance of the capacitor are equal, which leads to a value of

$u = 1$ . This leads to an attenuation  $\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{2}}$  and a phase of  $\phi = -\frac{\pi}{4} = -45^\circ$ .

### 1.3 Log-Log Plots

Often you will see the attenuation of a filter on a log-log graph, ie the log of the attenuation against the log of the frequency. This is usually because the frequency can cover many powers of ten, and the attenuation can get very low very fast.

First we'll start by taking the logarithm of equation 1.8

$$\begin{aligned} \ln \left| \frac{V_{out}}{V_{in}} \right| &= \ln \left( \frac{1}{\sqrt{1+u^2}} \right) \\ A &= -\frac{1}{2} \ln (1+u^2) \end{aligned} \quad (1.13)$$

where we have let  $A = \ln \left| \frac{V_{out}}{V_{in}} \right|$ . Now if we let  $U = \ln u$ .

$$\begin{aligned} u &= \exp U \\ u^2 &= \exp U \times \exp U = \exp (2U) \end{aligned} \quad (1.14)$$

putting equation 1.3 into equation 1.14 gives us

$$A = -\frac{1}{2} \ln [1 + \exp (2U)] \quad (1.15)$$

Now expanding  $u$  to get a relationship to  $f$ .

$$\begin{aligned} u &= 2\pi RCf \\ \ln u &= \ln (2\pi RCf) \\ U &= \ln (2\pi RC) + \ln f \end{aligned} \quad (1.16)$$

Substituting in equation 1.16 into equation 1.15 gives

$$\begin{aligned} A &= -\frac{1}{2} \ln [1 + \exp (2 \ln (2\pi RC) + 2F)] \\ &= -\frac{1}{2} \ln [1 + \exp (k + x)] \end{aligned} \quad (1.17)$$

where  $F = \ln f$ ,  $k = 2 \ln(2\pi RC)$  and  $x = 2F$ . We will plot this function later, but it's interesting to look at the derivative of equation 1.17.

$$\begin{aligned}
\frac{dA}{dx} &= -\frac{1}{2} \frac{d}{dx} (\ln [1 + \exp(k+x)]) \\
&= -\frac{1}{2} \frac{dw}{dx} \frac{d}{dw} (\ln w) \\
&= -\frac{1}{2} \frac{\exp(k+x)}{1 + \exp(k+x)} \\
&= -\frac{1}{2} \frac{1}{1 + \exp(-(k+x))} \\
&= -\frac{1}{2} S(k+x)
\end{aligned} \tag{1.18}$$

with  $w = 1 + \exp(k+x)$  and  $S(x)$  is the sigmoid function which is defined as  $S(x) = \frac{1}{1+\exp(-x)}$ . Then to get  $\frac{dA}{dF}$  it's a simple matter of the chain rule.

$$\begin{aligned}
\frac{dA}{dF} &= \frac{dA}{dx} \frac{dx}{dF} \\
\frac{dA}{dF} &= -\frac{1}{2} S(k+x) \times 2 \\
\frac{dA}{dF} &= -S(k+2F)
\end{aligned} \tag{1.19}$$

Looking back at equation 1.17 again

$$A = -\frac{1}{2} \ln [1 + \exp(k+2F)] \tag{1.20}$$

where  $F = \ln f$  and  $k = 2 \ln(2\pi RC)$ . We can simplify this with the following result

$$\begin{aligned}
\ln(a+b) &= \ln \left( a \left( 1 + \frac{b}{a} \right) \right) \\
&= \ln a + \ln \left( 1 + \frac{b}{a} \right)
\end{aligned} \tag{1.21}$$



If we take  $a = \exp(k + 2F)$  and  $b = 1$  from equation 1.17 in equation 1.21 we get

$$\begin{aligned}
 -\frac{1}{2} \ln(\exp(k + 2F) + 1) &= -\frac{1}{2} \ln(\exp(k + 2F)) - \frac{1}{2} \ln\left(1 + \frac{1}{\exp(k + 2F)}\right) \\
 &= -\frac{1}{2} [\ln(\exp(k + 2F))] - \frac{1}{2} \ln\left(1 + \frac{1}{\exp(k + 2F)}\right)
 \end{aligned}
 \tag{1.22}$$