
FILTERS

NOTES ON PASSIVE ELECTRIC FILTER CIRCUITS

Hannah Michelle Ellis

June 2, 2020

Contents

| | | |
|---|--------------------|---|
| 1 | RC Low Pass Filter | 2 |
|---|--------------------|---|

List of Tables

List of Figures

| | | |
|---|---|---|
| 1 | Circuit diagram for a RC low pass filter. | 2 |
|---|---|---|

1 RC Low Pass Filter

A simple low pass filter can be formed from a resistor and a capacitor in series.

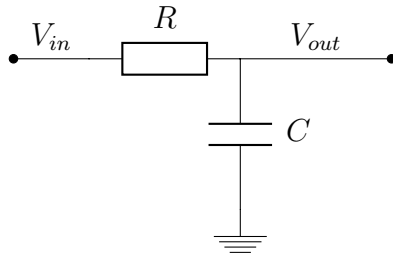


Figure 1: Circuit diagram for a RC low pass filter.

We can see from figure 1, that the output voltage is the same as the voltage across the capacitor. So we have

$$\begin{aligned} V_{in} &= V_R + V_C \\ &= IR + V_{out} \end{aligned} \tag{1.1}$$

Using the fact that the current through the RC section of the circuit is given by

$$I = \frac{V_{in}}{R - iX_C} \tag{1.2}$$

Leading to the output voltage being

$$\begin{aligned} V_{out} &= V_{in} - IR \\ &= V_{in} - \frac{V_{in}R}{R - iX_C} \\ &= V_{in} \left[1 - \frac{V_{in}R}{R - iX_C} \right] \end{aligned} \tag{1.3}$$

which leads to a ratio of the output voltage to the input voltage

of

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= 1 - \frac{R}{R - iX_C} \\ &= \frac{-iX_C}{R - iX_C} \\ &= \frac{-iX_C(R + iX_C)}{R^2 + X_C^2}\end{aligned}\tag{1.4}$$

Now if we let

$$u = \frac{R}{X_C} = \omega RC\tag{1.5}$$

we can see that $R = uX_C$, and putting this in equation 1.4 leads to

$$\frac{V_{out}}{V_{in}} = \frac{-iX_C^2(u + i)}{u^2X_C^2 + X_C^2}\tag{1.6}$$

$$= \frac{1 - iu}{1 + u^2}\tag{1.7}$$

Summary

We looked at the classic example of a low pass RC filter circuit, and discovered the relationship between the voltage into the filter and the voltage out of the filter is given by

$$\frac{V_{out}}{V_{in}} = \frac{1 - iu}{1 + u^2}$$

where $u = \frac{R}{X_C} = \omega RC$.

We can work out the magnitude and the phase angle of the

attenuation through the filter as follows.

$$\begin{aligned}\left|\frac{V_{out}}{V_{in}}\right| &= \sqrt{\frac{1-iu}{1+u^2} \frac{1+iu}{1+u^2}} \\ &= \frac{\sqrt{1+u^2}}{1+u^2} \\ &= \frac{1}{\sqrt{1+u^2}}\end{aligned}\tag{1.8}$$