

Transistor Circuits

Hannah Ellis

October 5, 2023

Contents

1	Basic Common Emitter circuit	1
---	------------------------------	---

1 Basic Common Emitter circuit

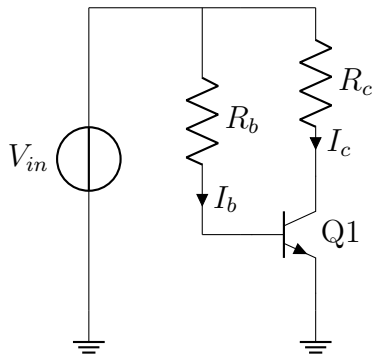


Figure 1: Basic Common Emitter Circuit

For a transistor in forward active mode, we can use the approximation

$$I_c = \beta I_b \quad (1.1)$$

We can use the fact that the voltage drop across a resistor divided by it's resistance is the current that flows through it to get

$$\frac{V_{in} - V_{ce}}{R_c} = \beta \frac{V_{in} - V_{be}}{R_b} \quad (1.2)$$