
FILTERS

NOTES ON PASSIVE ELECTRIC FILTER CIRCUITS

Hannah Michelle Ellis

June 4, 2020

Contents

1	RC Low Pass Filter	2
1.1	Filter Attenuation	2
1.1.1	Cutoff Frequency	2
1.1.2	Attenuation revisited	3
1.2	Log-Log Form	5

List of Tables

List of Figures

1	Circuit diagram for a RC low pass filter.	2
---	---	---

1 RC Low Pass Filter

1.1 Filter Attenuation

A simple low pass filter can be formed from a resistor and a capacitor in series.

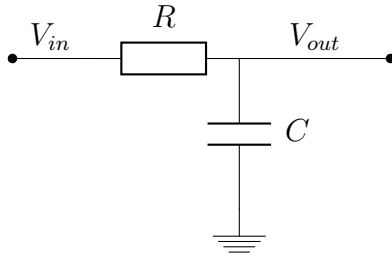


Figure 1: Circuit diagram for a RC low pass filter.

We can see from figure 1, that the circuit forms a potential divider just with a reactive element instead of purely resistive. The attenuation is then given by the standard potential divider result

$$\frac{V_{out}}{V_{in}} = \frac{-iX_C}{R - iX_C} \quad (1.1)$$

1.1.1 Cutoff Frequency

Let's introduce a new variable called u , where

$$\begin{aligned} u &= \frac{R}{X_C} \\ &= \omega RC \end{aligned} \quad (1.2)$$

where $\omega = 2\pi f$. If we look at the frequency when the resulting $u = 1$, which we will label f_0 or ω_0

$$\begin{aligned} \omega_0 RC &= 1 \\ \omega_0 &= \frac{1}{RC} \end{aligned} \quad (1.3)$$

We call the frequency when $u = 1$ the *cutoff frequency*, for reasons that will be clear later on. This frequency is when the resistance of the resistor is equal to the reactance of the capacitor¹ You can see that we can use the cutoff frequency as a replacement for our RC value, in equation 1.2.

$$\begin{aligned} u &= \omega RC \\ &= \frac{\omega}{\omega_0} = \frac{f}{f_0} \end{aligned} \tag{1.4}$$

1.1.2 Attenuation revisited

Now we have some understanding of the variable we introduced u , we can substitute it into our equation for the attenuation (equation 1.1), by noting that from equation 1.2 $R = uX_C$

$$\begin{aligned} \frac{V_{\text{out}}}{V_{\text{in}}} &= \frac{-iX_C}{R - iX_C} \\ &= \frac{-iX_C}{uX_C - iX_C} \\ &= \frac{-i}{u - i} \\ &= \frac{1 - iu}{u^2 + 1} \end{aligned} \tag{1.5}$$

Normally, we don't consider the attenuation as a complex value, instead we care more about the magnitude and phase shift of an attenuation.

$$\begin{aligned} \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| &= \frac{\sqrt{1 + u^2}}{1 + u^2} \\ &= \frac{1}{\sqrt{1 + u^2}} \\ &= \frac{1}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}} \end{aligned} \tag{1.6}$$

¹by equal here, we mean the magnitudes are equal. If not the phase shift.

Where we have used equation 1.4 in place of u . For the phase shift of the filter,

$$\phi = -\arctan u = -\arctan \frac{f}{f_0} \quad (1.7)$$

Summary

In the last section we discovered the cutoff frequency was given by

$$f_0 = \frac{1}{2\pi RC}$$

and that the ratio of resistance to reactance can be given by

$$u = \frac{R}{X_C} = 2\pi RCf = \frac{f}{f_0}$$

and that the attenuation of the filter is given by

$$\begin{aligned} \frac{V_{\text{out}}}{V_{\text{in}}} &= \frac{-iX_C}{R - iX_C} \\ &= \frac{1 - iu}{u^2 + 1} \end{aligned}$$

or in terms of magnitude and phase shift

$$\begin{aligned} \left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| &= \frac{1}{\sqrt{1 + u^2}} \\ &= \frac{1}{\sqrt{1 + \left(\frac{f}{f_0}\right)^2}} \end{aligned}$$

$$\phi = -\arctan u = -\arctan \frac{f}{f_0}$$

1.2 Log-Log Form

You won't often see attenuation given in the form seen earlier. It is more likely to be seen in Log-Log form, due to wanting to see the behaviour over a large range of frequencies and the fact the attenuation itself can get very small very fast. However it helps to look at the logarithm of u before looking at the attenuation straight away.

$$\ln u = \ln \frac{f}{f_0} = \ln f - \ln f_0 = F - F_0 \quad (1.8)$$

where we have used $F = \ln f$ and $F_0 = \ln f_0$